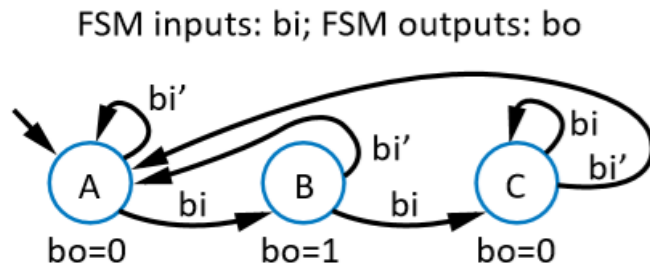



1. Decide states and draw the state diagram for your FSM controller.

State Diagram for Synchronizer:



(chapter 3/page47)

State Diagram for The Game:

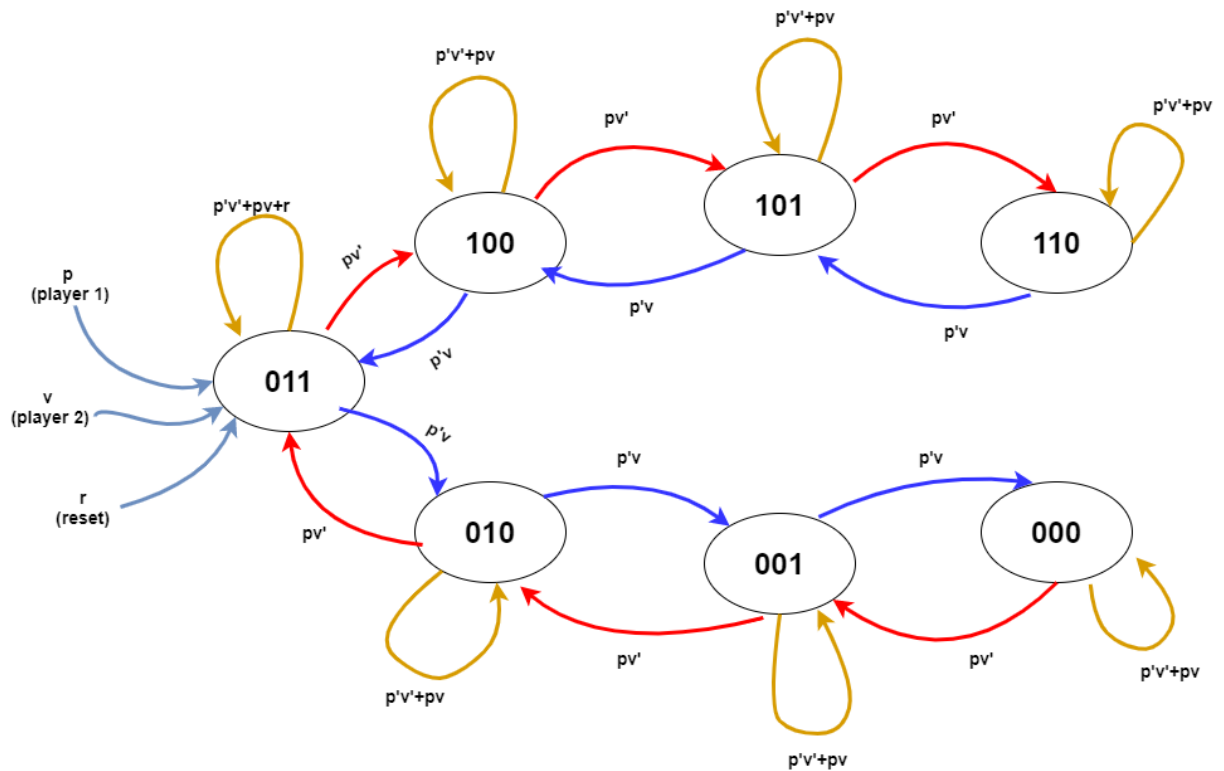

2. Draw truth table.

1	S2	S1	S0	p	v	r	n2	n1	n0
2	0	0	0	0	0	0	0	0	0
3	0	0	0	0	0	1	0	1	1
4	0	0	0	0	1	0	0	0	0
5	0	0	0	0	1	1	0	1	1
6	0	0	0	1	0	0	0	0	1
7	0	0	0	1	0	1	0	1	1
8	0	0	0	1	1	0	0	0	0
9	0	0	0	1	1	1	0	1	1
10	0	0	1	0	0	0	0	0	1
11	0	0	1	0	0	1	0	1	1
12	0	0	1	0	1	0	0	0	0
13	0	0	1	0	1	1	0	1	1
14	0	0	1	1	0	0	0	1	0
15	0	0	1	1	0	1	0	1	1
16	0	0	1	1	1	0	0	0	1
17	0	0	1	1	1	1	0	1	1
18	0	1	0	0	0	0	0	1	0
19	0	1	0	0	0	1	0	1	1
20	0	1	0	0	1	0	0	0	1
21	0	1	0	0	1	1	0	1	1
22	0	1	0	1	0	0	0	1	1
23	0	1	0	1	0	1	0	1	1
24	0	1	0	1	1	0	0	1	0
25	0	1	0	1	1	1	0	1	1
26	0	1	1	0	0	0	0	1	1
27	0	1	1	0	0	1	0	1	1
28	0	1	1	0	1	0	0	1	0
29	0	1	1	0	1	1	0	1	1
30	0	1	1	1	0	0	1	0	0
31	0	1	1	1	0	1	0	1	1
32	0	1	1	1	1	0	0	1	1
33	0	1	1	1	1	1	0	1	1
34	1	0	0	0	0	0	1	0	0
35	1	0	0	0	0	1	0	1	1
36	1	0	0	0	1	0	0	1	1
37	1	0	0	0	1	1	0	1	1
38	1	0	0	1	0	0	1	0	1
39	1	0	0	1	0	1	0	1	1
40	1	0	0	1	1	0	1	0	0
41	1	0	0	1	1	1	0	1	1
42	1	0	1	0	0	0	1	0	1
43	1	0	1	0	0	1	0	1	1
44	1	0	1	0	1	0	1	0	0
45	1	0	1	0	1	1	0	1	1
46	1	0	1	1	0	0	1	1	0
47	1	0	1	1	0	1	0	1	1
48	1	0	1	1	1	0	1	0	1
49	1	0	1	1	1	1	0	1	1
50	1	1	0	0	0	0	1	1	0
51	1	1	0	0	0	1	0	1	1
52	1	1	0	0	1	0	1	0	1
53	1	1	0	0	1	1	0	1	1
54	1	1	0	1	0	0	1	1	0
55	1	1	0	1	0	1	0	1	1
56	1	1	0	1	1	0	1	1	0
57	1	1	0	1	1	1	0	1	1
58	1	1	1	x	x	x	-	-	-

3. Derive Boolean expressions from the truth table.


$$n2 = (s1 \ s0 \ p \ \sim v \ \sim r) + (s2 \ \sim v \ \sim r) + (s2 \ p \ \sim r) + (s2 \ s0 \ \sim r) + (s2 \ s1 \ \sim r)$$

$$n1 = (r) + (\sim s1 \ s0 \ p \ \sim v) + (s1 \ \sim s0 \ \sim v) + (s1 \ p \ v) + (s1 \ s0 \ \sim p) + (s2 \ \sim s1 \ \sim s0 \ \sim p \ v)$$

$$n0 = (r) + (\sim s2 \ \sim s0 \ p \ \sim v) + (\sim s1 \ \sim s0 \ p \ \sim v) + (s0 \ \sim p \ \sim v) + (s0 \ p \ v) + (s1 \ \sim s0 \ \sim p \ v) + (s2 \ \sim s0 \ \sim p \ v)$$

Note: Because of the complexity of truth table, boolean expressions are derived from different online calculators.

4. Draw the circuit on Logisim.

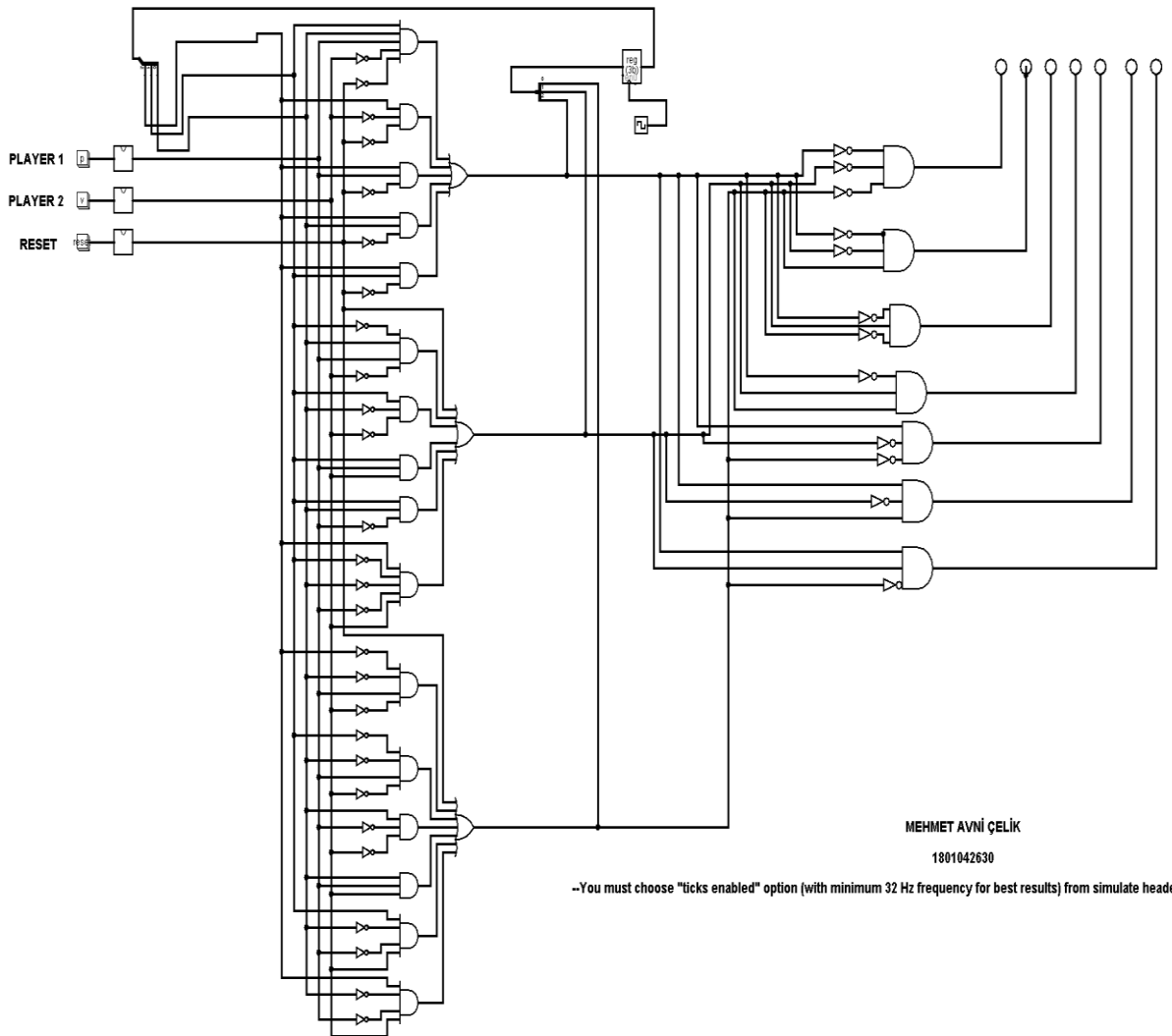

5.)

- No glitch/error was observed in the designed circuit.